

# Analog IC Lab #1

Hatem Mohamed Ahmed Rashed 20010447  
Ziad Amr Ibrahim Mohamed 20010637

## 1 Practical Results

### 1.1 Unity Gain Amplifier

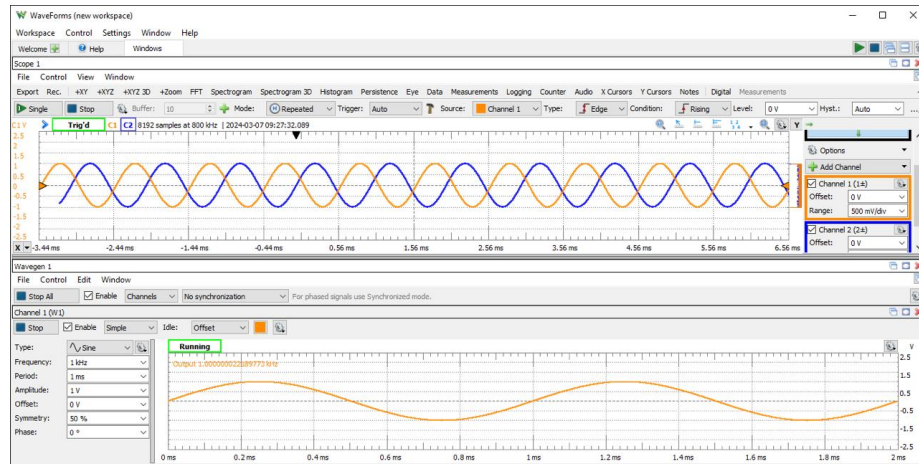


Figure 1: The practical result plot for Unity Gain Amplifier

## 1.2 Non Inverting Amplifier with Gain of 2

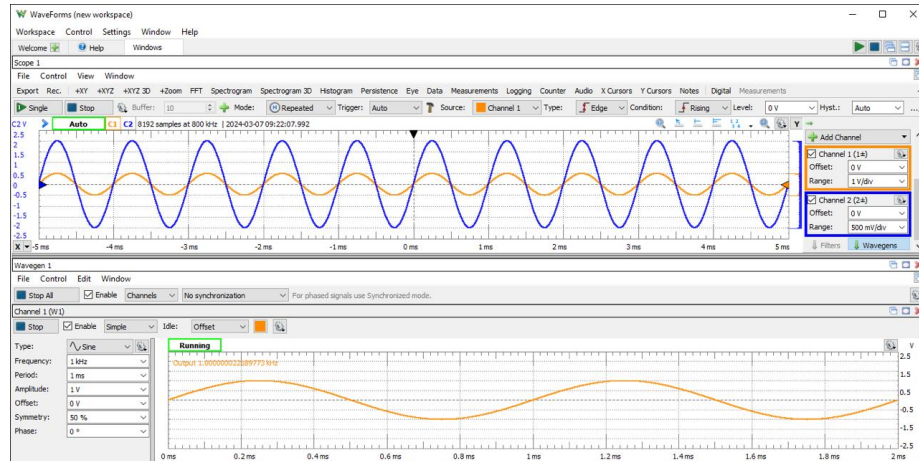


Figure 2: The practical result plot for Non Inverting Amplifier with Gain of 2

## 1.3 Inverting Amplifier with Gain of 2.2

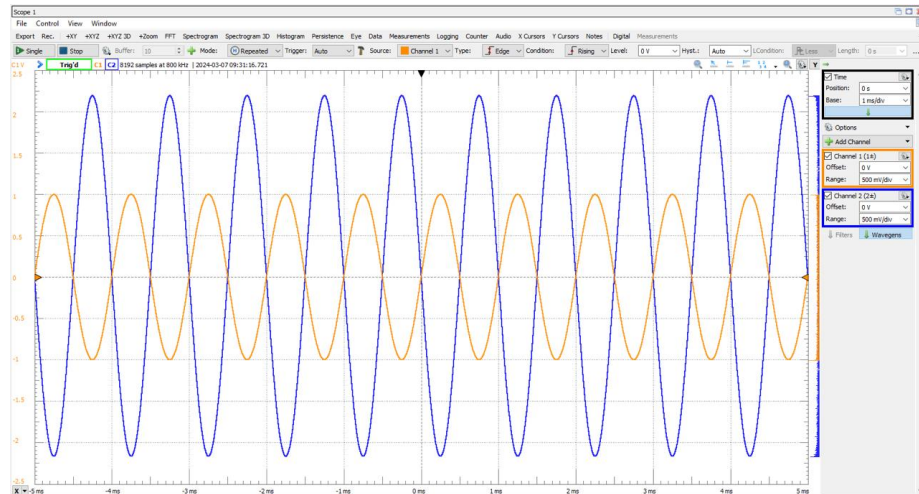


Figure 3: The practical result plot for Inverting Amplifier with Gain of 2.2

## 2 Simulation Results

### 2.1 Unity Gain Amplifier

#### 2.1.1 Unity Sine Gain

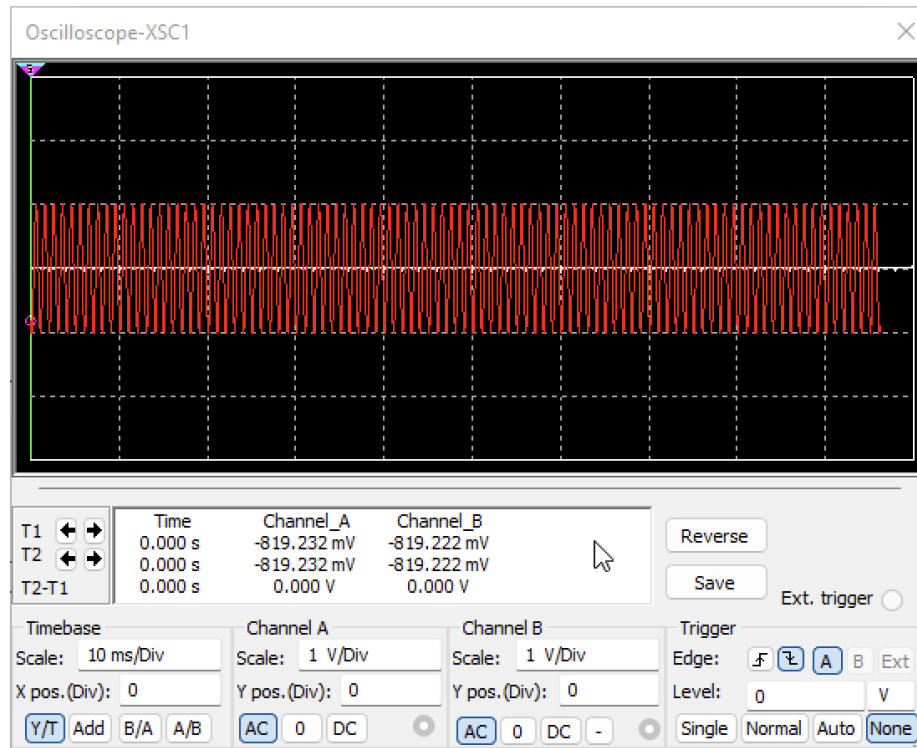


Figure 4: The simulation plot for Unity Sine Gain

### 2.1.2 Unity Sine Frequency

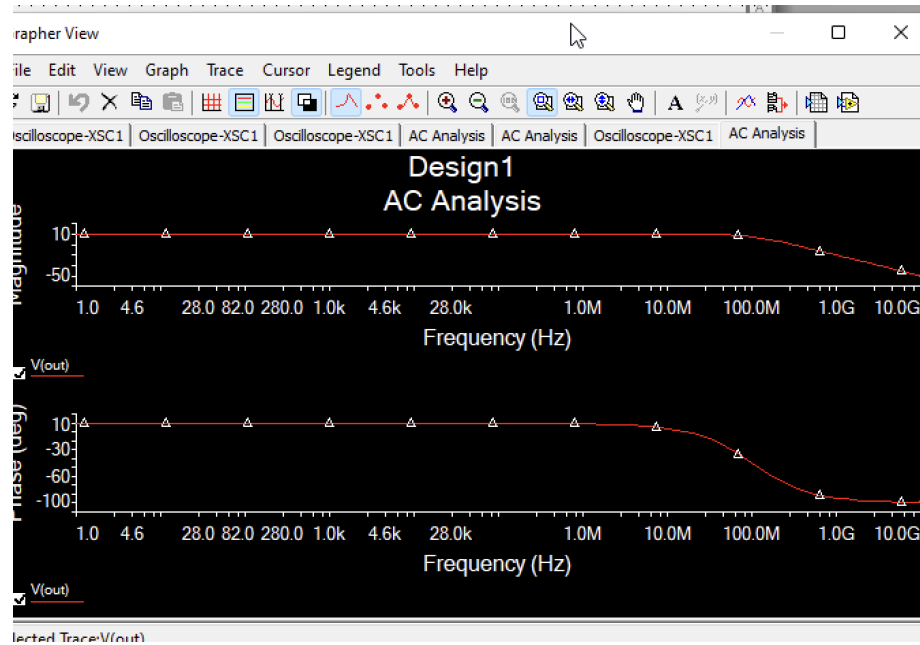


Figure 5: The simulation plot for Unity Sine Freq

### 2.1.3 Unity Square Gain

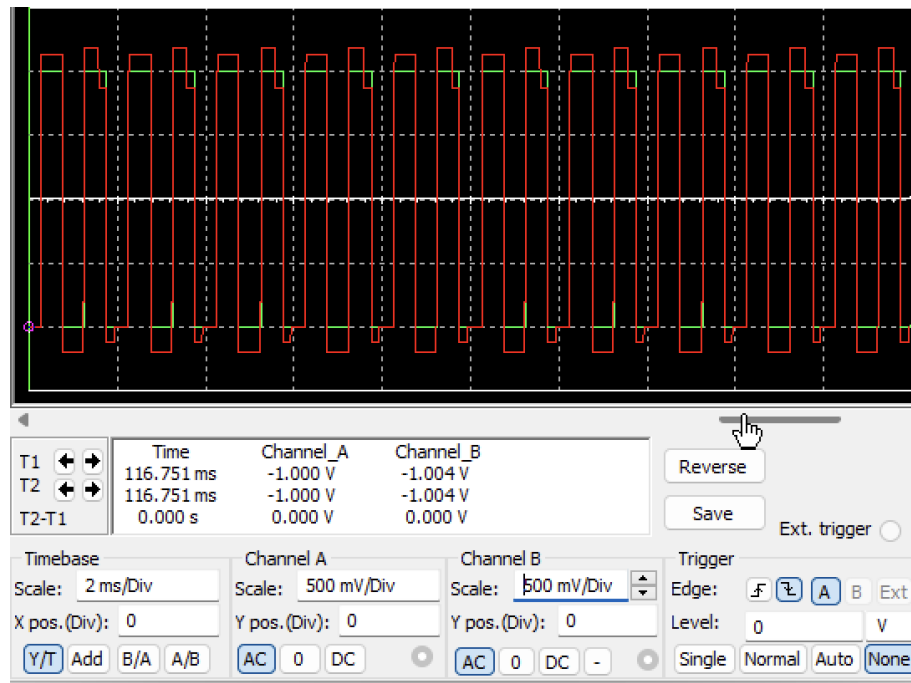


Figure 6: The simulation plot for unity Unity Square Gain

### 2.1.4 Unity Square Frequency

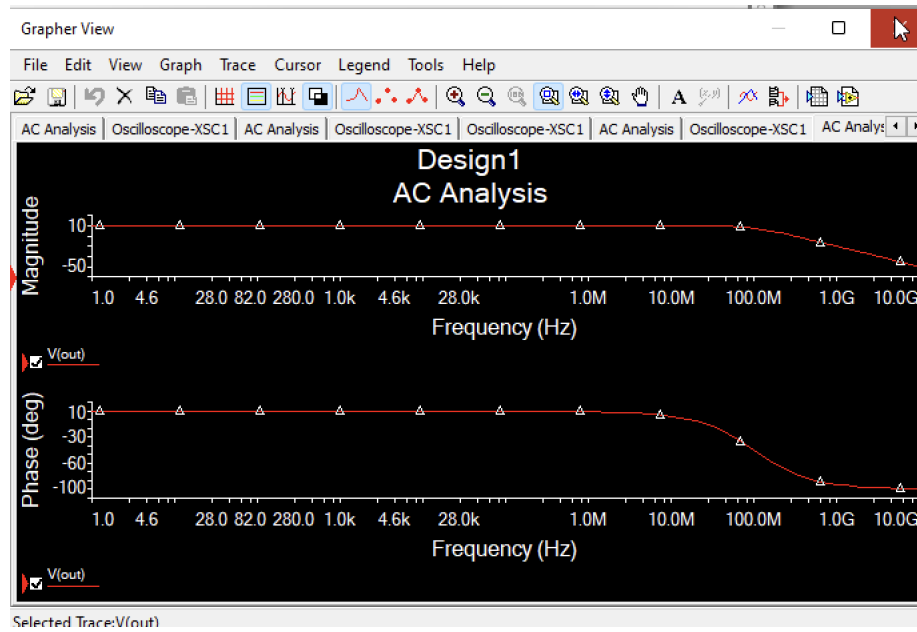


Figure 7: The simulation plot for Unity Square Freq

## 2.2 Non Inverting Amplifier

### 2.2.1 Non Inverting Amplifier Circuit

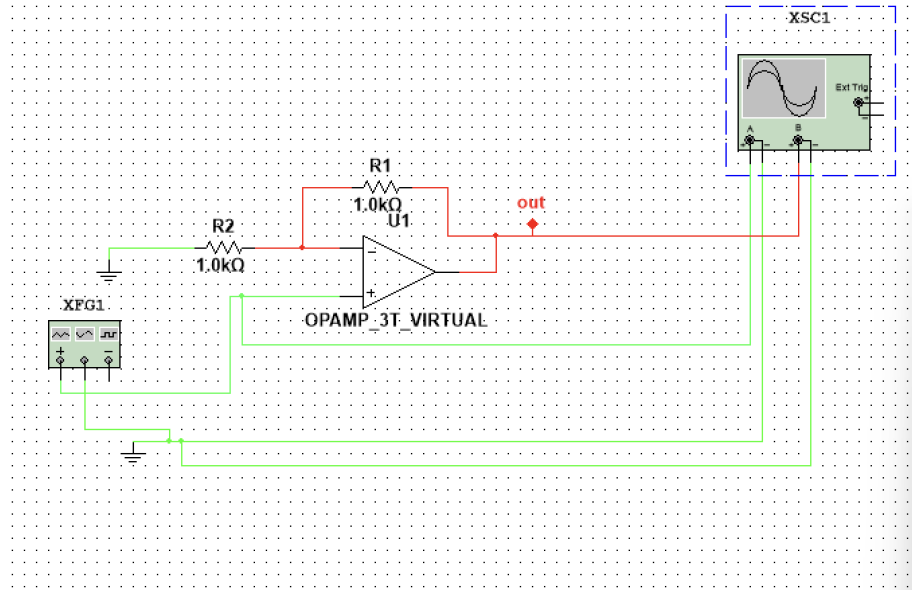


Figure 8: The simulation plot for Non Inverting Amplifier circuit

## 2.2.2 Non Inverting Amplifier Sine Gain

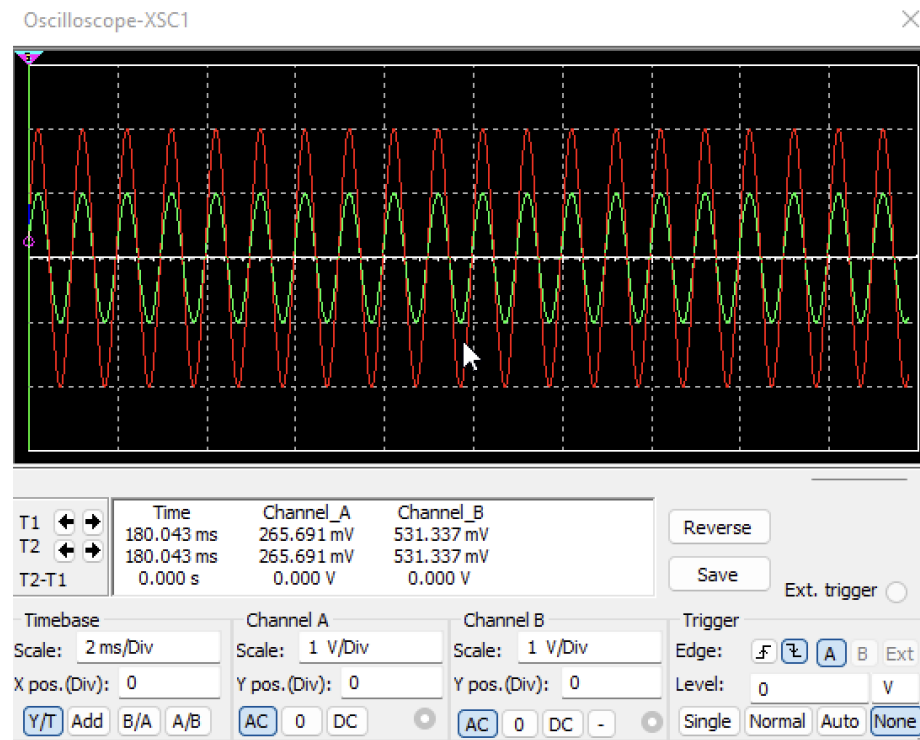


Figure 9: The simulation plot for Non Inverting Amplifier Sine Gain



### 2.2.3 Non Inverting Amplifier Sine Frequency

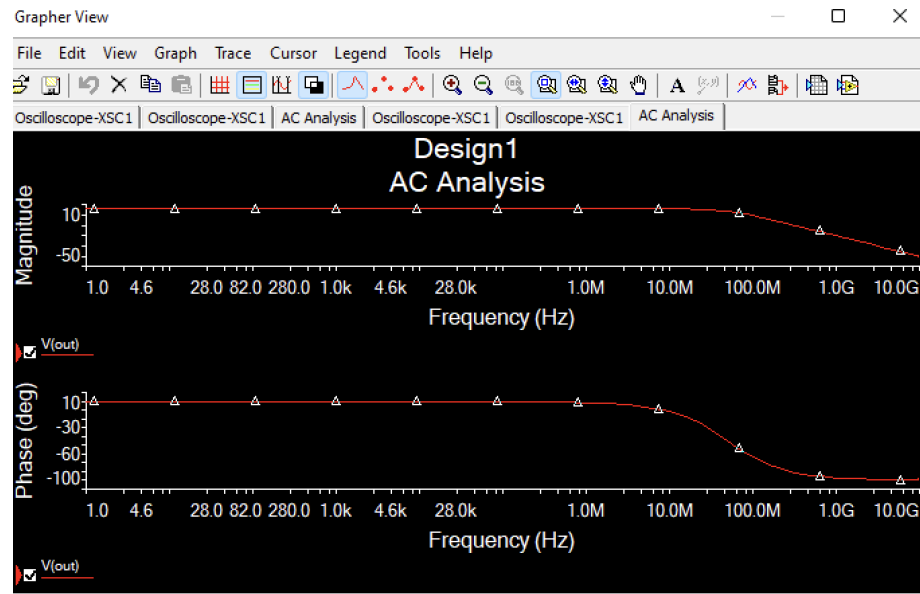


Figure 10: The simulation plot for Non Inverting Amplifier Square Gain

## 2.2.4 Non Inverting Amplifier Square Gain

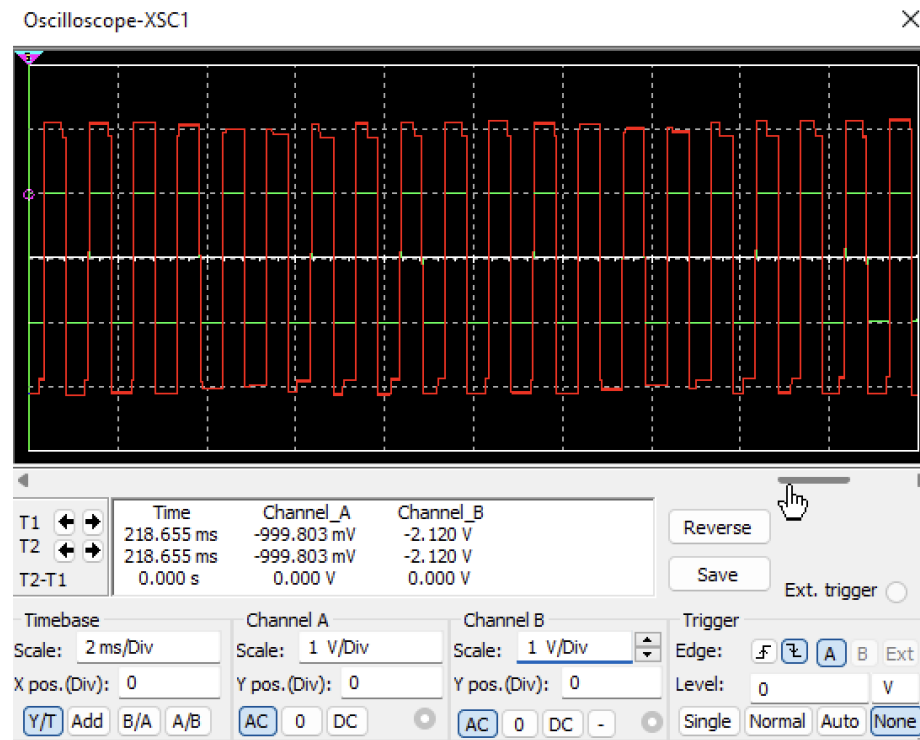


Figure 11: The simulation plot for Non Inverting Amplifier Square Gain

### 2.2.5 Non Inverting Amplifier Square Frequency

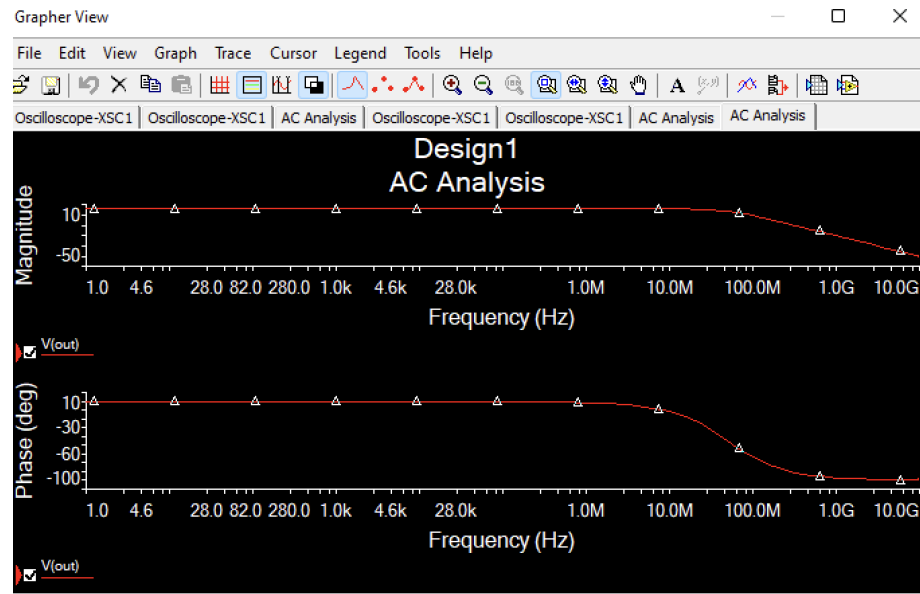


Figure 12: The simulation plot for Non Inverting Amplifier Square Frequency

## 2.3 Inverting Amplifier

### 2.3.1 Inverting Amplifier Circuit

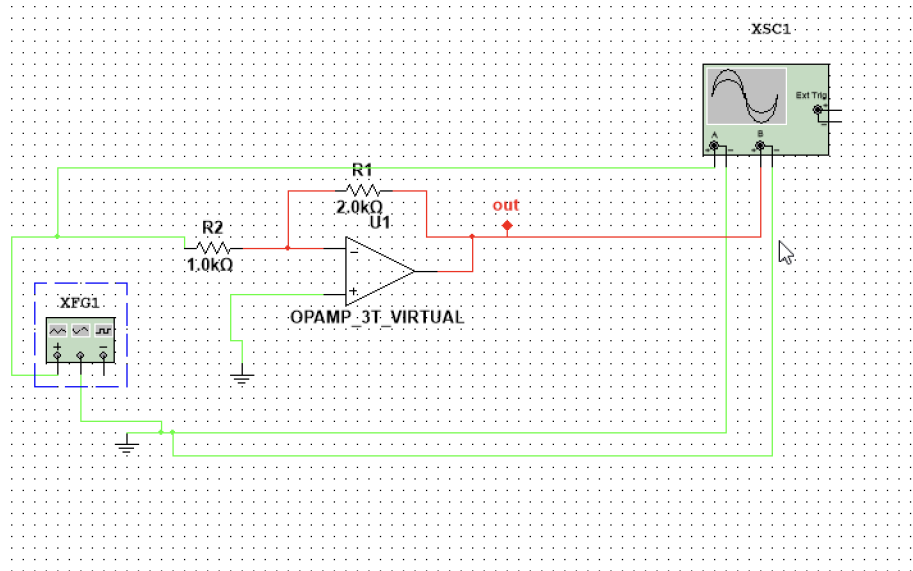


Figure 13: The simulation plot for Inverting Amplifier circuit

### 2.3.2 Inverting Amplifier Sine Gain

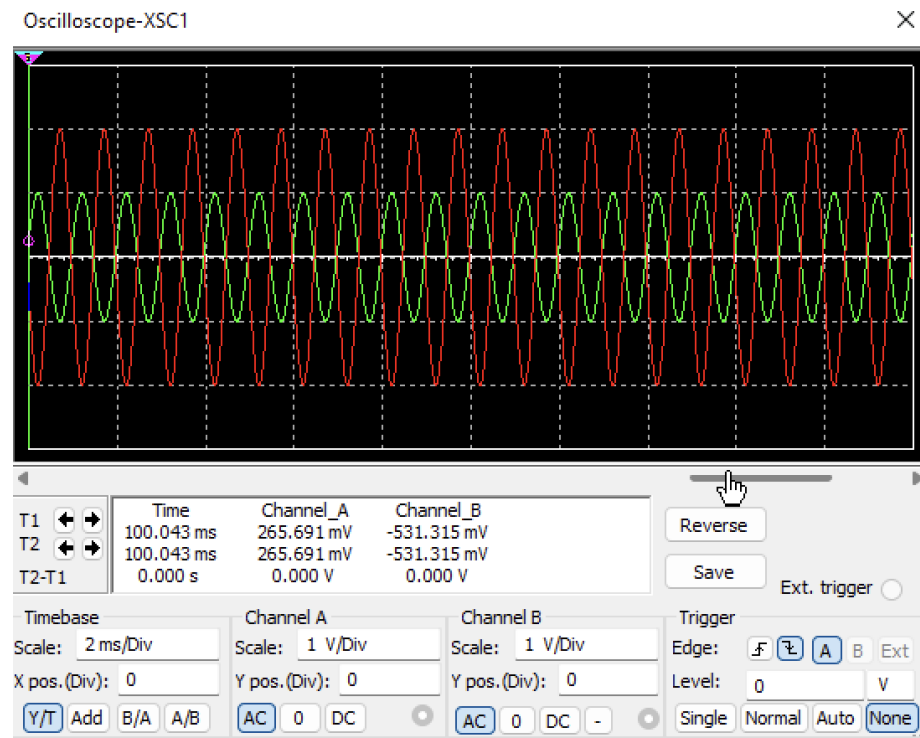


Figure 14: The simulation plot for Inverting Amplifier Sine Gain

### 2.3.3 Inverting Amplifier Sine Frequency

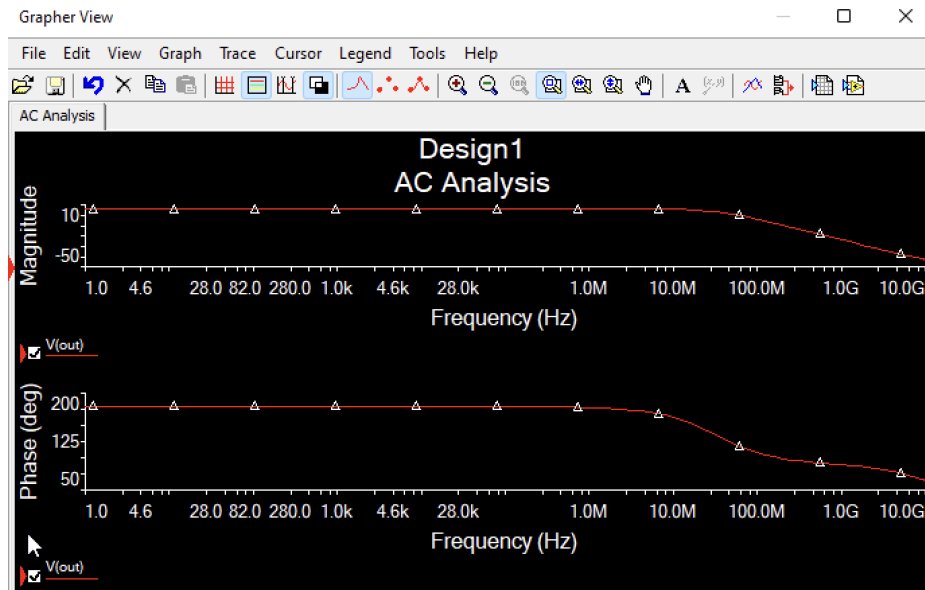


Figure 15: The simulation plot for Inverting Amplifier Square Gain

### 2.3.4 Inverting Amplifier Square Gain

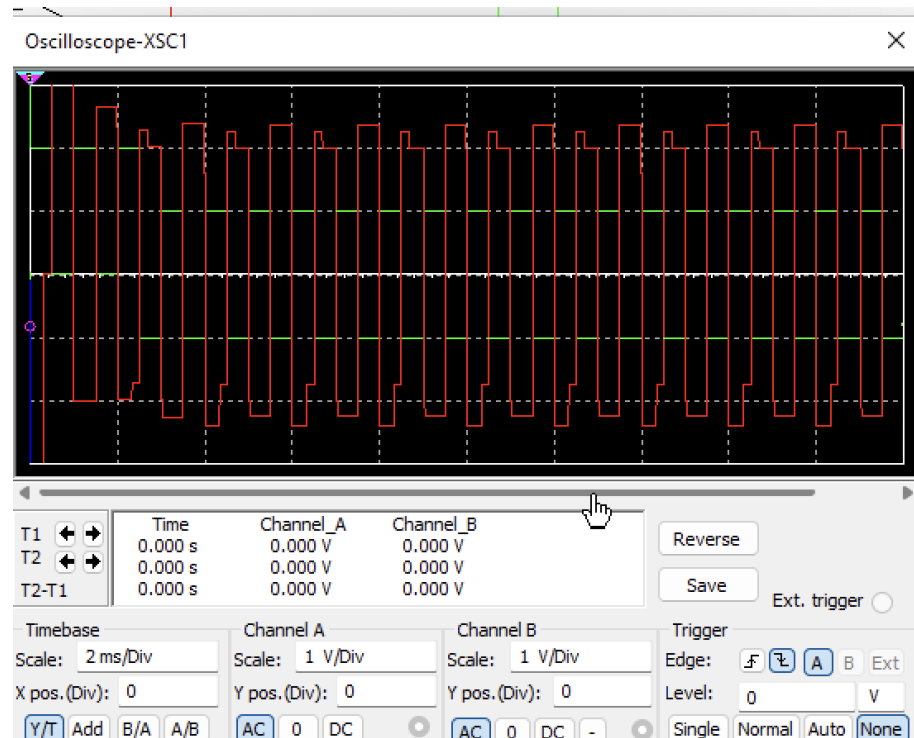


Figure 16: The simulation plot for Inverting Amplifier Square Gain

### 2.3.5 Inverting Amplifier Square Frequency

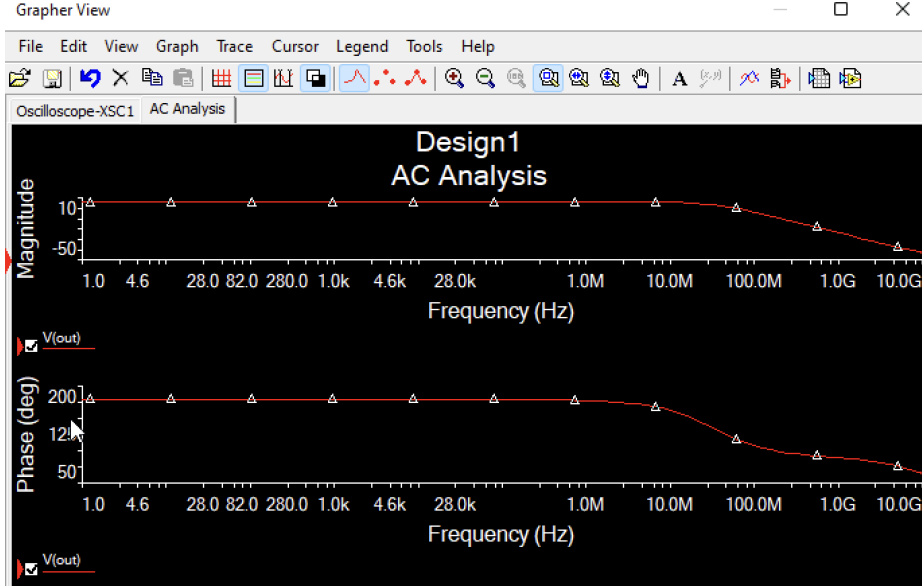


Figure 17: The simulation plot for Inverting Amplifier Square Frequency

## 3 Instrumentation Amplifier

### 3.1 instrumentation Amplifier with gain of 3

#### 3.1.1 Procedures

the procedures taken for this experment are to get a gain of 3

$$V_{input1} = 1volt, \quad Freq_{input1} = 1kHz \quad (1)$$

$$V_{input2} = 1.5volt, \quad Freq_{input2} = 1kHz \quad (2)$$

$$A_v = \left(1 + \frac{2R}{R * n}\right) * \frac{R}{R} = 3 \quad (3)$$



### 3.1.2 instrumentation Amplifier Circuit with input sine wave

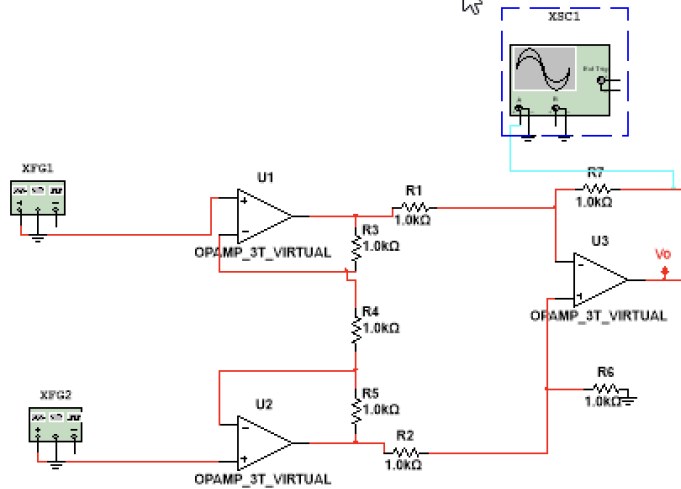


Figure 18: The simulation plot for instrumentation Amplifier Circuit with input sine wave

### 3.1.3 Output

#### 3.1.4 instrumentation Amplifier output

$$V_{out} = (1.5 - 1) * 3 = 1.5volts \quad (4)$$

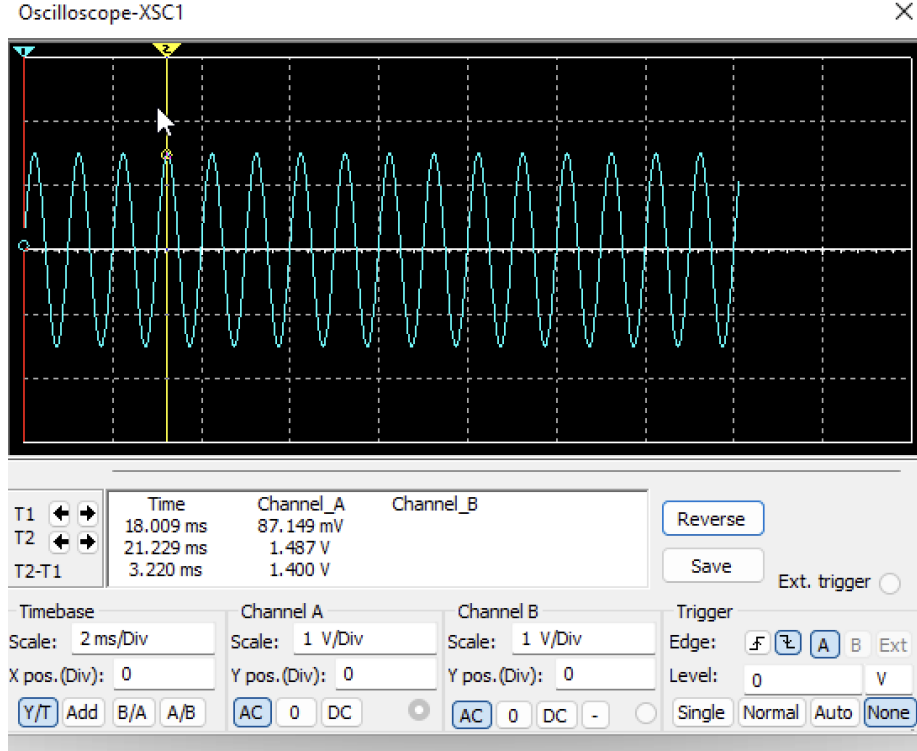


Figure 19: The simulation plot for instrumentation Amplifier Square output

## 3.2 instrumentation Amplifier with gain of 5

### 3.2.1 Procedures

the procedures taken for this experment are to get a gain of 5

$$V_{input1} = 1volt, \quad Freq_{input1} = 1kHz \quad (5)$$

$$V_{input2} = 1.5volt, \quad Freq_{input2} = 1kHz \quad (6)$$

$$A_v = \left(1 + \frac{R}{R} + \frac{2R}{R * n}\right) = 5 \quad (7)$$

### 3.2.2 instrumentation Amplifier Circuit with input sine wave

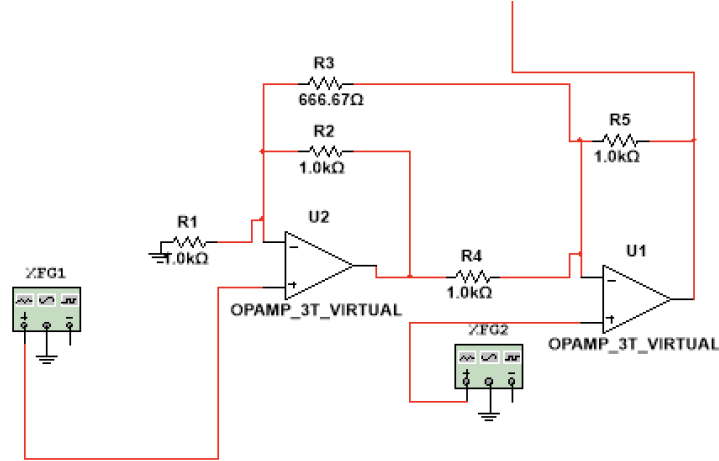


Figure 20: The simulation plot for instrumentation Amplifier Circuit with input sine wave

### 3.2.3 Output

#### 3.2.4 instrumentation Amplifier output

$$V_{out} = (1.5 - 1) * 5 = 2.5volts \quad (8)$$

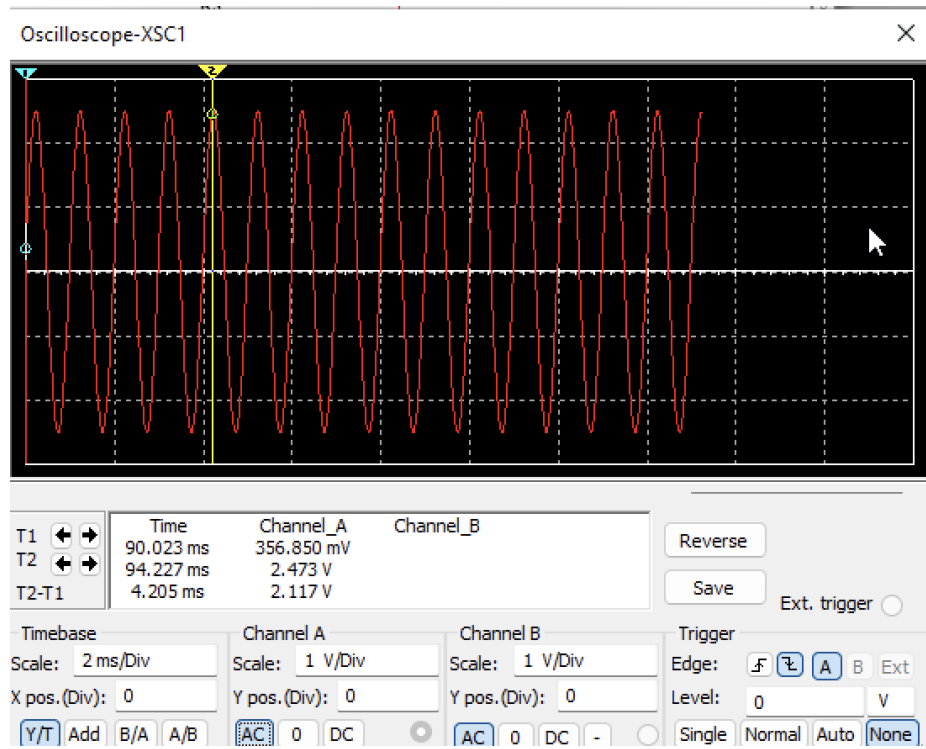


Figure 21: The simulation plot for instrumentation Amplifier Square output